

# Electricity Class 12

## Problems Based on the Given Formulae

### 1. Calculate Current:

- A charge of 10 C flows through a conductor in 2 seconds. Calculate the current.
- Formula:  $I = \frac{Q}{t}$

### 2. Ohm's Law:

- A resistor has a resistance of 5  $\Omega$  and a current of 2 A flows through it. Find the voltage across the resistor.
- Formula:  $V = IR$

### 3. Drift Velocity:

- Calculate the drift velocity if the number density of free electrons in a copper wire is  $8.5 \times 10^{28}$  electrons/m<sup>3</sup>, the cross-sectional area is  $1 \times 10^{-6}$  m<sup>2</sup>, and the current is 3 A.
- Formula:  $I = neAv_d$

### 4. Resistance and Resistivity:

- A wire of length 2 m and cross-sectional area  $1 \times 10^{-6}$  m<sup>2</sup> has a resistivity of  $1.7 \times 10^{-8}$   $\Omega \cdot m$ . Calculate its resistance.
- Formula:  $R = \frac{\rho l}{A}$

### 5. Relation for Resistivity:

- Given the number density  $n$ , the charge of an electron  $e$ , relaxation time  $\tau$ , and mass of electron  $m$ , derive the resistivity of a material.
- Formula:  $\rho = \frac{m}{ne^2\tau}$

### 6. Conductance:

- Find the conductance of a resistor with resistance 10  $\Omega$ .
- Formula:  $C = \frac{1}{R}$

### 7. Current Density:

- If the current through a conductor is 5 A and the cross-sectional area is  $2 \times 10^{-6}$  m<sup>2</sup>, calculate the current density.
- Formula:  $J = \frac{I}{A}$

### 8. Mobility of Electron:

- Given the drift velocity  $v_d$  is  $5 \times 10^{-4}$  m/s and the electric field  $E$  is 10 V/m, calculate the mobility of the electron.
- Formula:  $\mu = \frac{v_d}{E}$

#### 9. Temperature Coefficient of Resistivity:

- A material has a resistivity of  $\rho_0 = 1.5 \times 10^{-8} \Omega \cdot m$  at  $T_0 = 20^\circ C$ . If the temperature coefficient of resistivity is  $\alpha = 0.0039^\circ C^{-1}$ , calculate the resistivity at  $100^\circ C$ .
- Formula:  $\rho = \rho_0[1 + \alpha(T - T_0)]$

#### 10. Finding Alpha:

- Given resistivities  $\rho_1$  and  $\rho_2$  at temperatures  $T_1$  and  $T_2$  respectively, find the temperature coefficient of resistivity  $\alpha$ .
- Formula:  $\alpha = \frac{\rho_2 - \rho_1}{\rho_1(T_2 - T_1)}$

#### 11. Series Combination:

- Calculate the equivalent resistance of three resistors  $R_1 = 2\Omega$ ,  $R_2 = 3\Omega$ , and  $R_3 = 4\Omega$  connected in series.
- Formula:  $R_s = R_1 + R_2 + R_3$

#### 12. Parallel Combination:

- Calculate the equivalent resistance of three resistors  $R_1 = 2\Omega$ ,  $R_2 = 3\Omega$ , and  $R_3 = 4\Omega$  connected in parallel.
- Formula:  $\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

#### 13. Electrical Power:

- A device operates at a voltage of 12 V and draws a current of 2 A. Calculate the power consumed by the device.
- Formula:  $P = VI$

#### 14. Internal Resistance:

- A cell with EMF  $E$  of 12 V has an internal resistance  $r$  of 1  $\Omega$ . When a resistor of 5  $\Omega$  is connected, calculate the terminal voltage.
- Formula:  $V = E - Ir$

#### 15. Internal Resistance Using Potentiometer:

- A potentiometer measures the potential drop across a known resistance  $R$ . Given  $l_1$  and  $l_2$  are the balancing lengths, calculate the internal resistance  $r$ .
- Formula:  $r = \left(\frac{l_1}{l_2} - 1\right)R$

#### 16. Current with Identical Cells in Series:

- Calculate the current drawn when  $n = 4$  identical cells, each with EMF  $E = 1.5V$  and internal resistance  $r = 0.5\Omega$ , are connected in series with an external resistance  $R = 10\Omega$ .
- Formula:  $I = \frac{nE}{R+nr}$

#### 17. Current with Cells in Parallel:

- Calculate the current drawn when  $m = 4$  cells are connected in parallel, each with EMF  $E = 1.5V$  and internal resistance  $r = 0.5\Omega$ , and the external resistance  $R = 2\Omega$ .
- Formula:  $I = \frac{mE}{(mR+r)}$

#### 18. Current with Rows of Identical Cells:

- Calculate the current drawn when  $m = 2$  rows of  $n = 3$  identical cells, each with EMF  $E = 1.5V$  and internal resistance  $r = 0.5\Omega$ , are connected with an external resistance  $R = 10\Omega$ .
- Formula:  $I = \frac{mnE}{mR+nr}$

#### 19. Kirchhoff's Junction Rule:

- Apply Kirchhoff's current law to a junction with three incoming currents  $I_1 = 2A$ ,  $I_2 = 3A$ , and one outgoing current  $I_3 = 4A$ . Calculate the unknown current.
- Formula:  $\sum I = 0$

#### 20. Balanced Condition of Wheatstone Bridge:

- In a Wheatstone bridge,  $P = 4\Omega$ ,  $Q = 6\Omega$ , and  $R = 3\Omega$ . Find the value of  $S$  for the bridge to be balanced.
- Formula:  $\frac{P}{Q} = \frac{R}{S}$

#### 21. Unknown Resistance Using Wheatstone Bridge:

- In a Wheatstone bridge, the known resistance  $R$  is  $5\Omega$ , and the balancing length  $l$  is  $40\text{ cm}$ . Calculate the unknown resistance  $S$ .
- Formula:  $S = \left(\frac{100-l}{l}\right)R$

#### 22. Potential Drop Using Potentiometer:

- A potentiometer wire has a length of  $1\text{ m}$  and a constant  $K = 0.01V/cm$ . Calculate the potential drop for a balancing length  $L$  of  $50\text{ cm}$ .
- Formula:  $V = KL$

#### 23. Comparison of EMFs Using Potentiometer:

- Two cells have EMFs  $E_1$  and  $E_2$ . Given the balancing lengths  $l_1 = 30\text{ cm}$  and  $l_2 = 45\text{ cm}$ , compare their EMFs.
- Formula:  $\frac{E_1}{E_2} = \frac{l_1}{l_2}$

These problems cover a range of concepts and formulae from the topic of current electricity, providing a comprehensive set of exercises for practice.