

# Electricity Class 12

## Key for the Problems

1.  $I = 5 \text{ A}$
2.  $V = 10 \text{ V}$
3.  $v_d = 2.21 \times 10^{-4} \text{ m/s}$
4.  $R = 3.4 \Omega$
5.  $\rho = \frac{m}{ne^2\tau}$
6.  $C = 0.1 \text{ S}$
7.  $J = 2.5 \times 10^6 \text{ A/m}^2$
8.  $\mu = 5 \times 10^{-5} \text{ m}^2/\text{V}\cdot\text{s}$
9.  $\rho = 1.122 \times 10^{-8} \Omega \cdot \text{m}$
10.  $\alpha = 0.0039 \text{ }^\circ\text{C}^{-1}$
11.  $R_s = 9 \Omega$
12.  $R_p = 0.92 \Omega$
13.  $P = 24 \text{ W}$
14.  $V = 10 \text{ V}$
15.  $r = 0.2 \Omega$
16.  $I = 0.45 \text{ A}$
17.  $I = 1 \text{ A}$
18.  $I = 0.6 \text{ A}$
19.  $I_4 = 1 \text{ A}$
20.  $S = 4.5 \Omega$
21.  $S = 7.5 \Omega$
22.  $V = 0.5 \text{ V}$
23.  $\frac{E_1}{E_2} = \frac{2}{3}$