




## ALTERNATING CURRENT

### Class 12 - Physics

**Time Allowed: 1 hour and 30 minutes**

**Maximum Marks: 46**

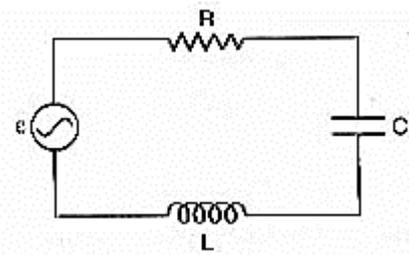
1. Show that the current leads the voltage in phase by  $\frac{\pi}{2}$  in an AC circuit containing an ideal capacitor. [3]
2. A series L-C-R circuit is connected to an AC source (200 V, 50 Hz). The voltages across the resistor, capacitor and inductor are respectively 200 V, 250 V and 250 V. [3]
  - i. The algebraic sum of the voltages across the three elements is greater than the voltage of the source. How is this paradox resolved?
  - ii. Given the value of the resistance of R is  $40\Omega$ . Calculate the current in the circuit.
3. A sinusoidal voltage of peak value 10 V is applied to a series LCR circuit in which resistance, capacitance, and inductance have values of  $10\Omega$ ,  $1\mu\text{F}$  and 1 H respectively. Find [3]
  - i. the peak voltage across the inductor at resonance
  - ii. quality factor of the circuit.
4. i. An LCR series circuit is connected to an ac source. If the angular resonant frequency of the circuit is  $\omega_0$ , will the current lead or lag behind or be in phase with the voltage when  $\omega < \omega_0$  and why? [3]
  - ii. We cannot step up a dc voltage using a transformer. Why?
  - iii. On what principle does a metal detector work?
5. Derive an expression for the impedance of an a.c. circuit with an inductor L and a resistor R in series. Also obtain the expression for average power in this circuit. [5]
6. A small town with a demand of 800 kW of electric power at 220 V is situated 15 km away from an electric plant generating power at 440 V. The resistance of the two wirelines carrying power is  $0.5\Omega$  per km. The town gets power from the line through a 4000 - 220 V step-down transformer at a sub-station in the town. [5]
  - a. Estimate the line power loss in the form of heat.
  - b. How much power must the plant supply, assuming there is negligible power loss due to leakage?
  - c. Characterize the step-up transformer at the plant.
7. i. Describe, with the help of a suitable diagram, the working principle of a step-up transformer. Obtain the relation between input and output voltages in terms of the number of turns of primary and secondary windings and the currents in the input and output circuits. [5]
  - ii. Given the input current 15 A and the input voltage of 100 V for a step-up transformer having 90% efficiency, find the output power and the voltage in the secondary if the output current is 3 A.
8. A series of LCR circuit is connected to a variable frequency 230 V source,  $L = 5.0\text{ H}$ ,  $C = 80\mu\text{F}$ ,  $R = 40\Omega$  [5]



- i. Determine the source frequency which drives the circuit in resonance.
- ii. Obtain the impedance of the circuit and the amplitude of current at the resonating frequency.
- iii. Determine the rms potential drops across the three elements of the circuit. Show that the potential drop across the LC combination is zero at the resonating frequency.

9. The power factor of the circuit shown in the figure is


[1]

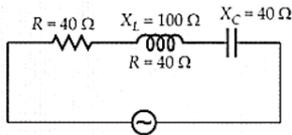

- |        |        |
|--------|--------|
| a) 0.2 | b) 0.6 |
| c) 0.8 | d) 0.4 |

10. If the reading of the voltmeter  $V_1$  is 40 V, then the reading of voltmeter  $V_2$  is

[1]

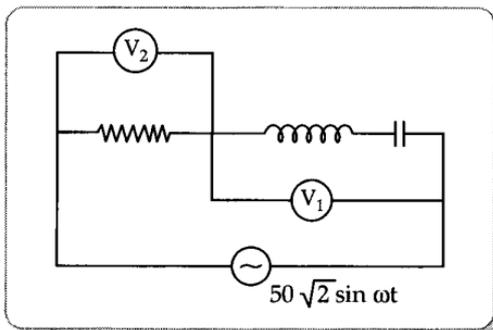


- |         |         |
|---------|---------|
| a) 15 V | b) 30 V |
| c) 58 V | d) 29 V |

11. A 50 Hz a.c. source of 20 V is connected across R and C as shown in the figure. The voltage across R is 12 V.

[1]

The voltage across C is

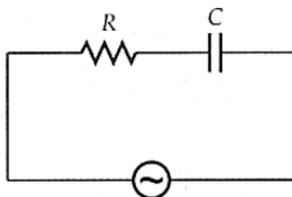

- |  |         |
|--|---------|
| a) not possible to determine, unless values of R and C are given | b) 10 V |
| c) 16 V  | d) 8 V  |

12. The rms value of potential difference V shown in the figure is

[1]



